


The background of the slide features a futuristic theme. On the left, a white and black robotic arm is shown in profile, reaching out towards the center. The background is composed of several elements: a series of white DNA double helix structures on the left, a row of grey server racks on the right, and a central purple band with white circular patterns. The text is overlaid on this purple band.

# ELEC1100: Introduction to Electro-Robot Design

## Lecture 5: IC and Pulse Generation



# ELEC1100 ROADMAP

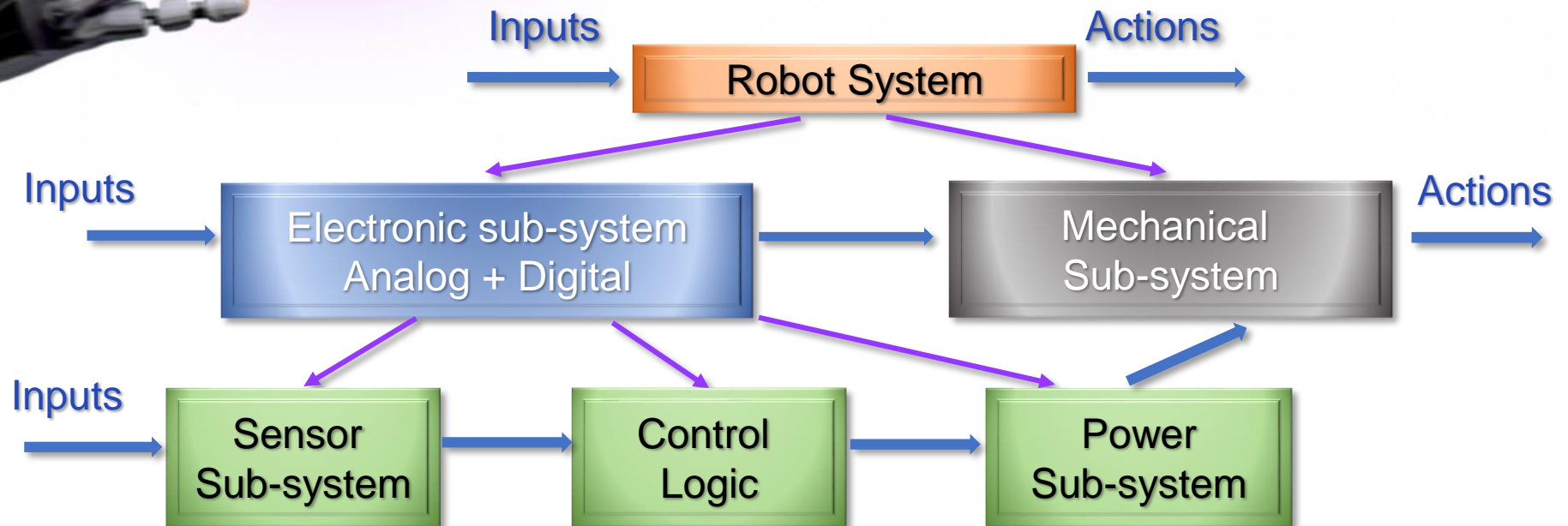

## Basic electronics:

- Wk1: Basic Electronics - Charge/Current/Voltage/Resistor
- Wk2: Energy/Power and DC Sources

## Motor Power Supply:


- Wk3: Pulse Signal and PWM Control




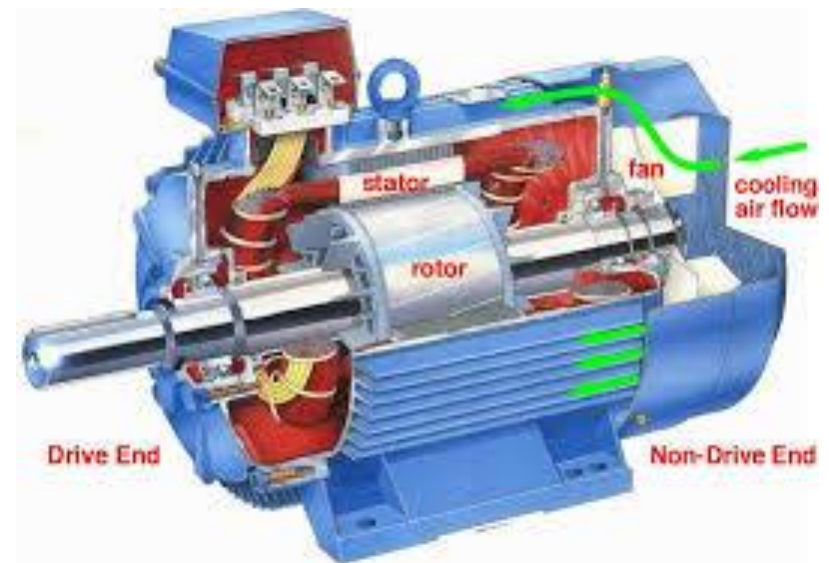
# WHAT ARE MOTORS?

- ❖ A motor is an electric-mechanical device, converting electricity to mechanical motion
- ❖ A revised energy conversion leads to a generator







# MAGNETIC BASICS

- ❖ A magnet has two poles: south and north
- ❖ Like poles repel, and opposite poles attract



(a)



(b)



(c)




(d)


Magnetic poles always come in pairs

Magnetic monopoles are predicted to exist but with no experimental evidence yet

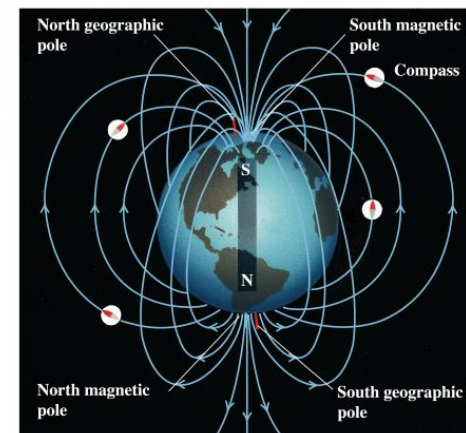The Earth's magnetic field appears to come from a giant bar magnet, but with its south pole located up near the Earth's north pole






Copyright © Addison Wesley Longman, Inc.

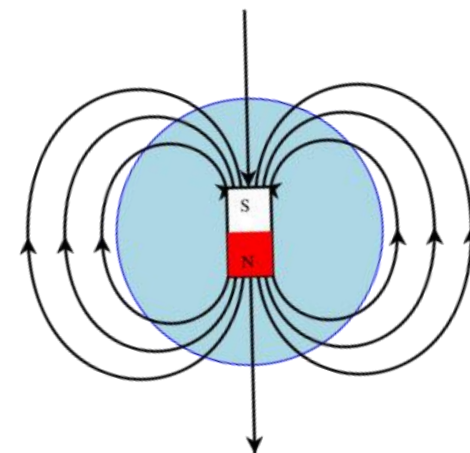


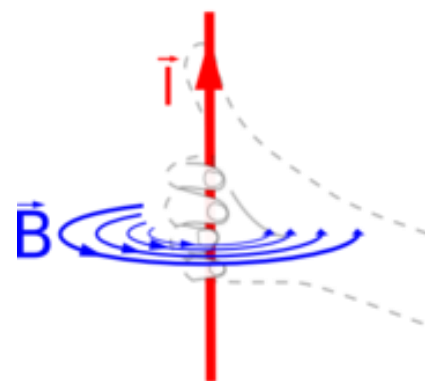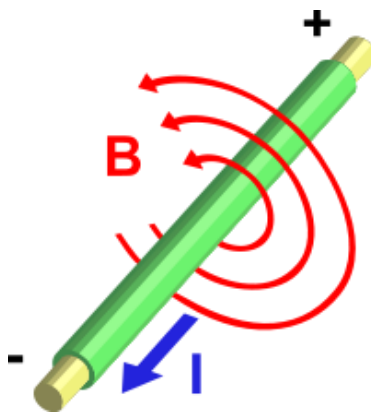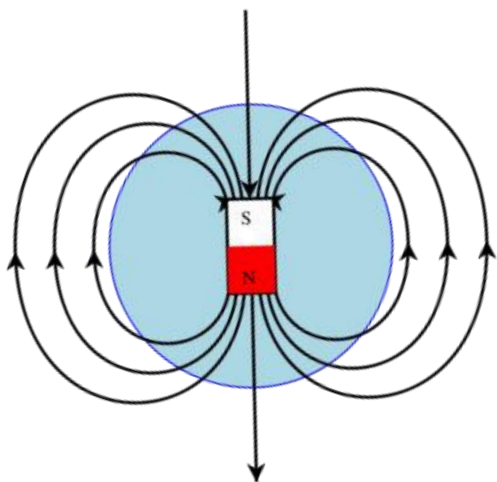
# CURRENT AND MAGNETIC FIELD

- ❖ A magnet produces a magnetic field from N to S
- ❖ A current flow through a wire also creates or “induces” a magnetic field (denoted by  $B$ )
- ❖ Direction of a B-field can be found by the right-hand-rule





**Right-Hand-Rule**


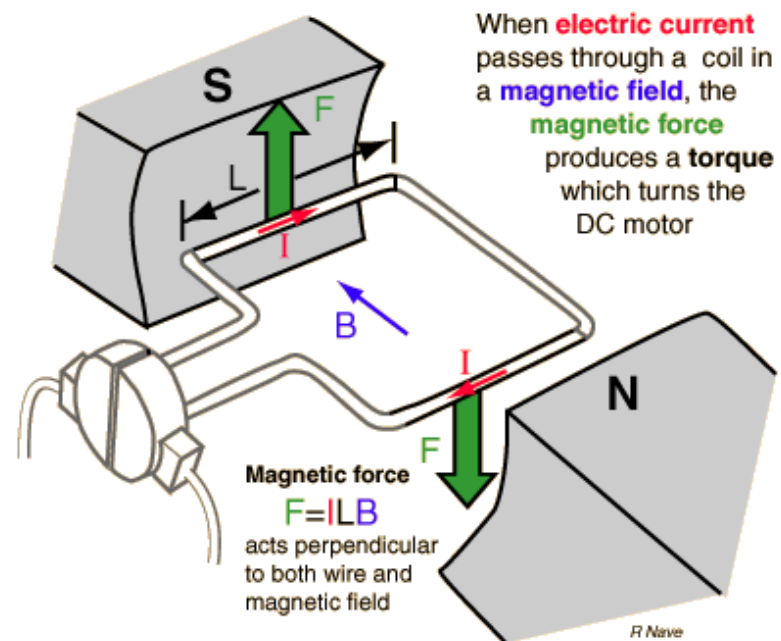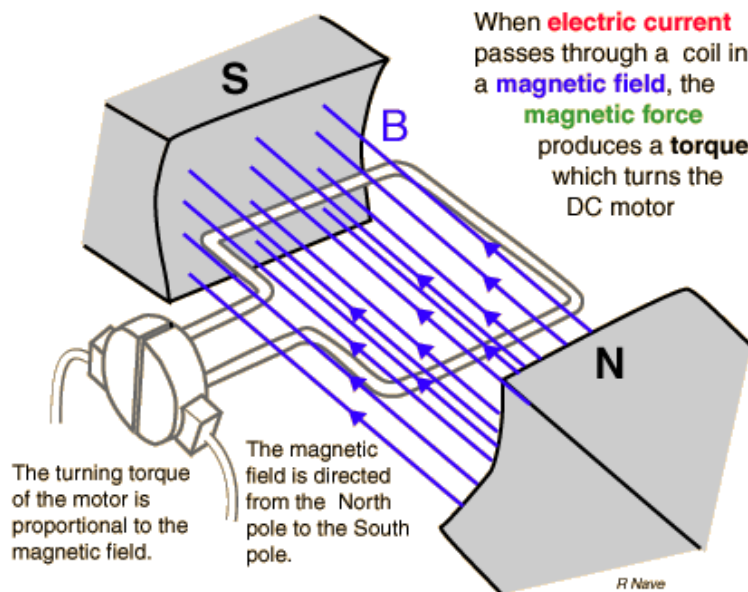
# ELECTRO-MAGNET INTERACTION

- ❖ When a wire carrying an electric current ( $I$ ) is placed in a magnetic field ( $B$ ), the wire will experience the Lorentz force








# MAGNETIC FORCE TO A CURRENT CARRYING WIRE


- ❖ Formula of the magnetic force on a current-carrying wire :

$$F = ILB \quad (B : \text{magnetic field } L : \text{wire Length } I : \text{current})$$

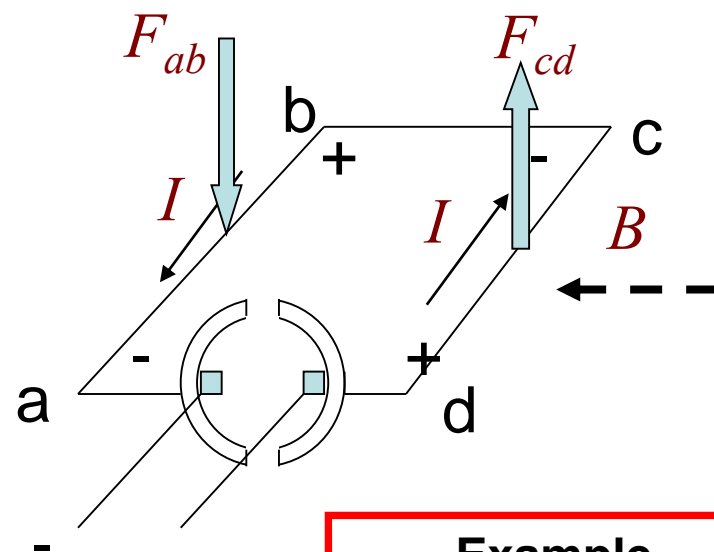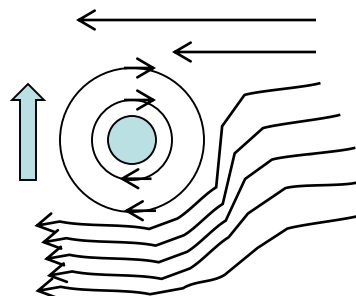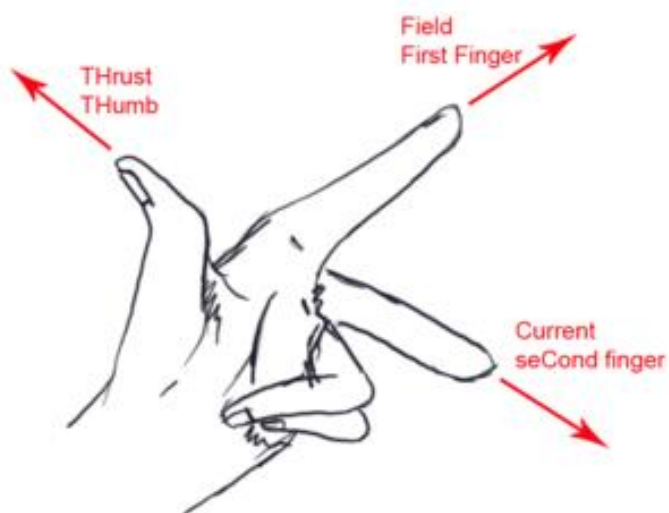- ❖ Direction of the force can be determined by the Fleming's Left-Hand-Rule




**Example**

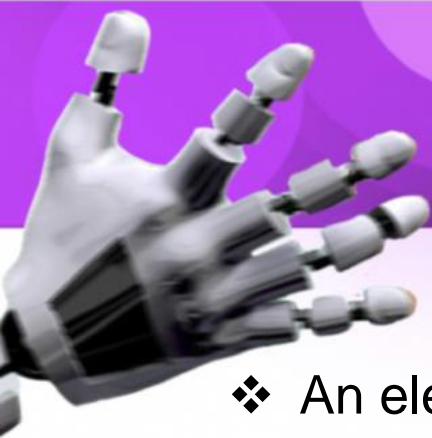

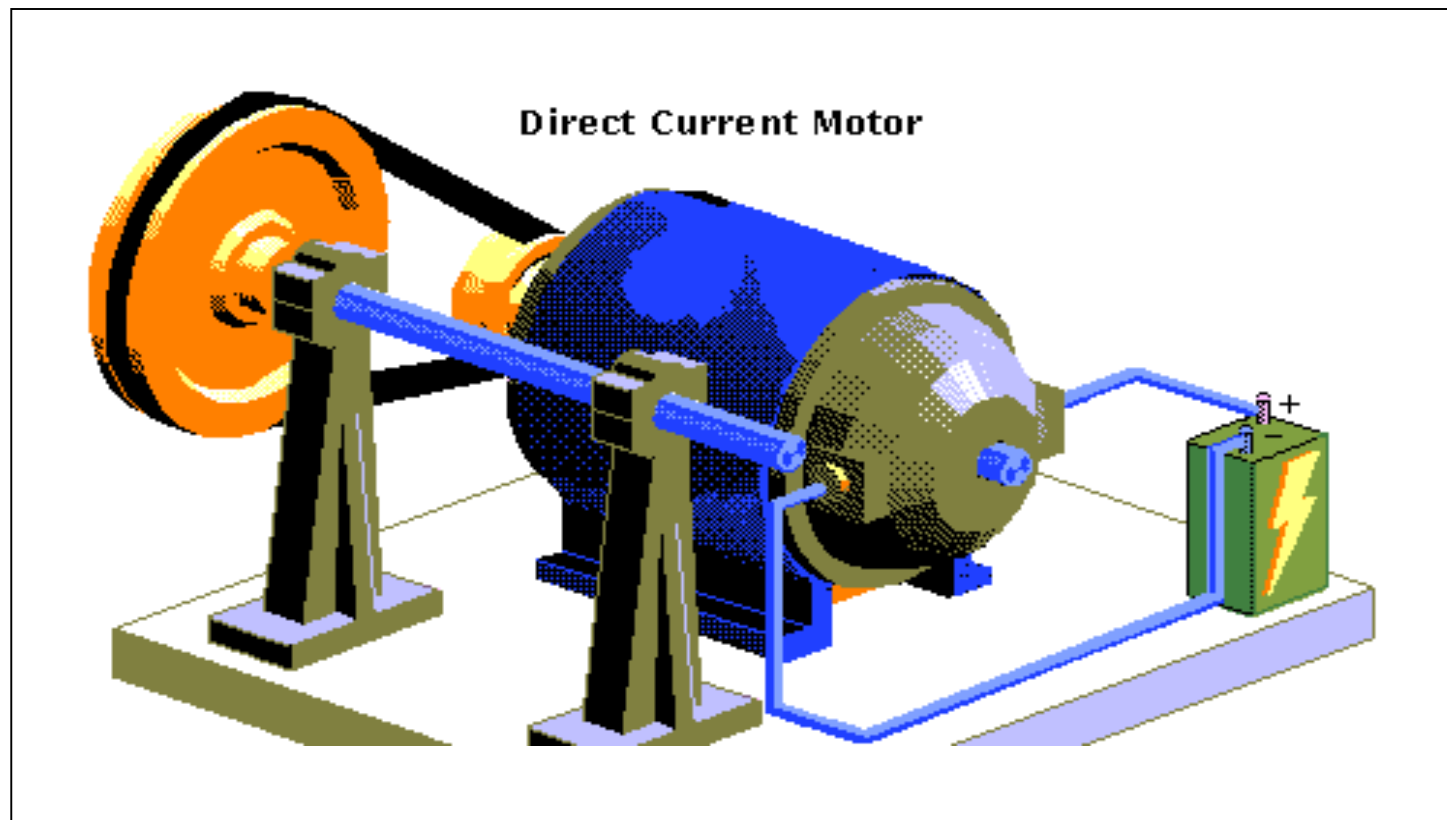
# ELECTRIC MOTOR

- ❖ An electric motor uses electrical energy to produce mechanical energy





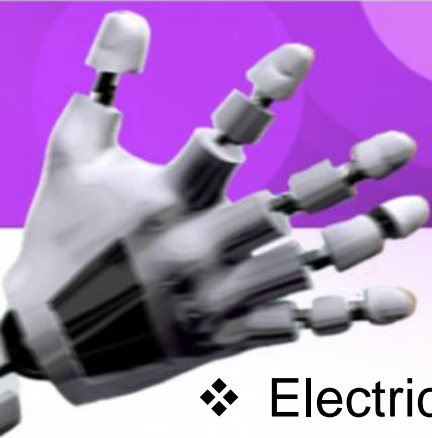

# ELECTRIC MOTOR

## ❖ Electric motor consists of two parts

- Stator: composed of two permanent magnet poles
- Rotor: composed of windings which are connected to a mechanical commutator

## ❖ Types of electric motors


- Brushed DC motor
- Brushless DC motor
- Stepper DC motor
- Micro motor
- ...




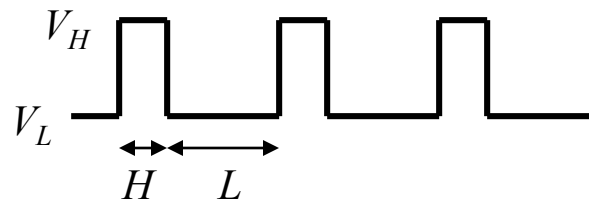
# PULSE GENERATION

- ❖ Mobile robots usually have DC voltage as power source
- ❖ Pulse voltage signal also has many applications that will be described in later lectures
- ❖ Can we generate pulses with desired timing out of a DC power supply?






# PULSE CHARACTERISTICS
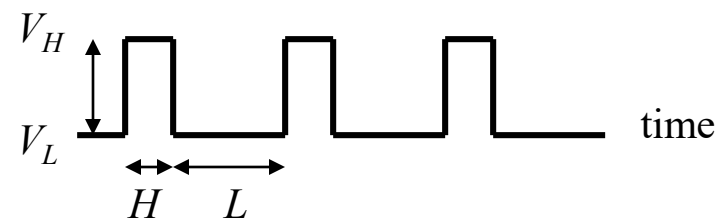
## ❖ Definition of terms

- A continuous well defined train of pulses sometimes also called a clock
- Clock high time =  $H$
- Clock low time =  $L$
- Clock period =  $T = H + L$
- Frequency =  $1/T$
- Duty cycle =  $H/T$
- Pulse height =  $V_H - V_L$





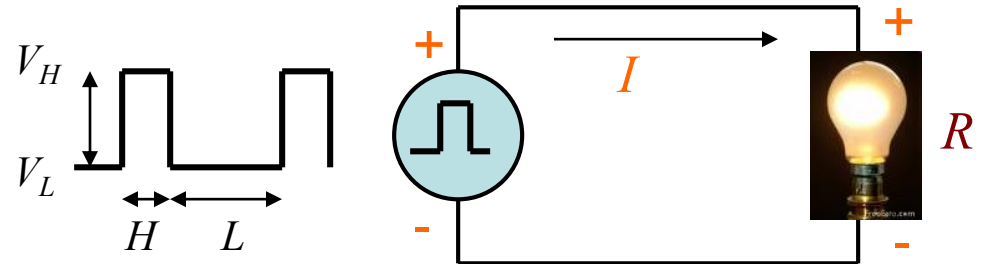
# AVERAGE VOLTAGE

- ❖ If you use a pulse to drive a load, what is the result?
- ❖ Average voltage

$$V_{ave} = \frac{H}{H+L} V_H + \frac{L}{H+L} V_L$$



➤ If  $V_L = 0$ , we have  $V_{ave} = \frac{H}{H+L} V_H$

- ❖ Is the brightness of the light equal to the circuit with the pulse voltage replaced by a battery with  $V = V_{ave}$ ?






# AVERAGE POWER AND EQUIVALENT VOLTAGE
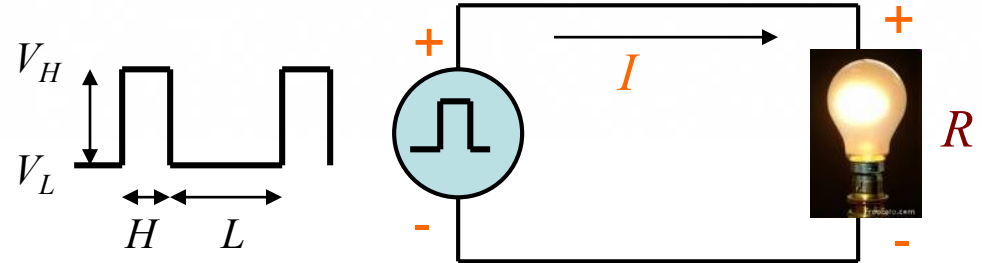
## ❖ Average Power

$$P_{ave} = \frac{H}{H+L} \frac{V_H^2}{R} + \frac{L}{H+L} \frac{V_L^2}{R}$$



- ❖ If the pulse voltage source is replaced by an equivalent DC voltage source with  $V = V_{eq}$ , we have:

$$P_{ave} = \frac{V_{eq}^2}{R}$$

- ❖ Equating the average power, we have

or if  $V_L = 0$

$$\frac{V_{eq}^2}{R} = \frac{H}{H+L} \frac{V_H^2}{R} + \frac{L}{H+L} \frac{V_L^2}{R} \Rightarrow V_{eq} = \sqrt{\frac{H}{H+L} V_H^2 + \frac{L}{H+L} V_L^2} \quad V_{eq} = \sqrt{\frac{H}{H+L}} V_H$$



# INTEGRATED CIRCUIT


- ❖ To generate pulses, you need to use a new component called **Integrated Circuit (IC)**.
- ❖ ICs can be made very compact in a fingernail size chip, having up to several billion transistors and other electronic components such as capacitors, resistors, diodes and etc.
- ❖ The particular IC you will use is **NE555**.
- ❖ The characteristics of an IC is given by the datasheet provided by the manufacturer.
- ❖ You will learn more ICs in future.




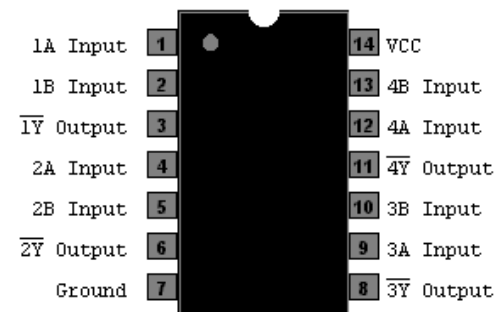
# IC CONNECTION

- ❖ Each IC has a **U-shape** mark or **a circle** to indicate its **top**




- ❖ After you identify the top of an IC, the pins are labeled starting with 1 from the top left corner going downward, then from the bottom right corner going upward


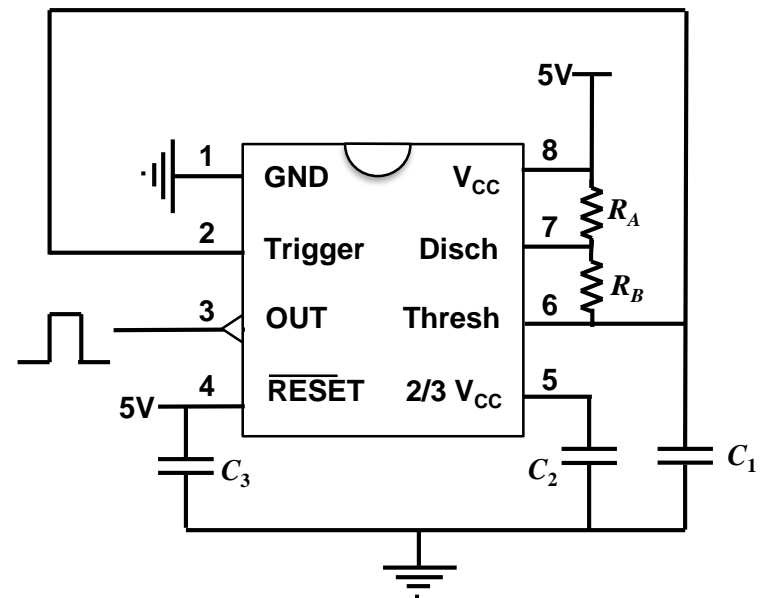
# CONSTRUCTING AN NE555 CIRCUIT

- ❖ NE555 application schematic
- ❖ Based on the datasheet, we have

- Clock high time =  $0.7(R_A + R_B)C_1$
- Clock low time =  $0.7R_B C_1$
- Clock period =  $0.7(R_A + 2R_B)C_1$
- Frequency =  $1/[0.7(R_A + 2R_B)C_1]$
- Duty cycle =  $(R_A + R_B)/(R_A + 2R_B)$








## EXERCISE: PULSE SIGNAL

❖ You are given a pulse below.

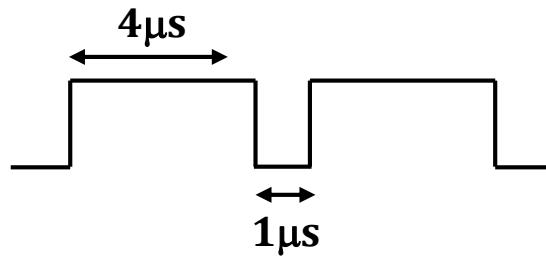

What is the value of its frequency?

$$\text{frequency} = 1/5\mu\text{s} = 200\text{kHz}$$









# RESISTOR TUNING

- ❖ Sometimes we want to adjust the value of a resistor to achieve certain power deliver
- ❖ A **variable resistor** can be used

C = control

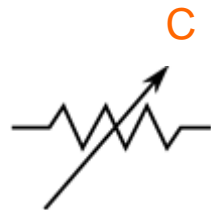

Symbol

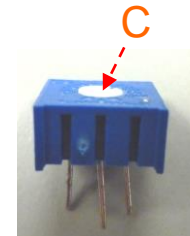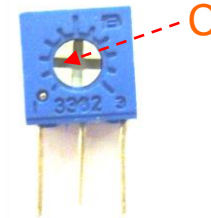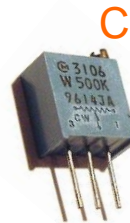


Real Object

- ❖ You will be using one of these in **Lab#03**


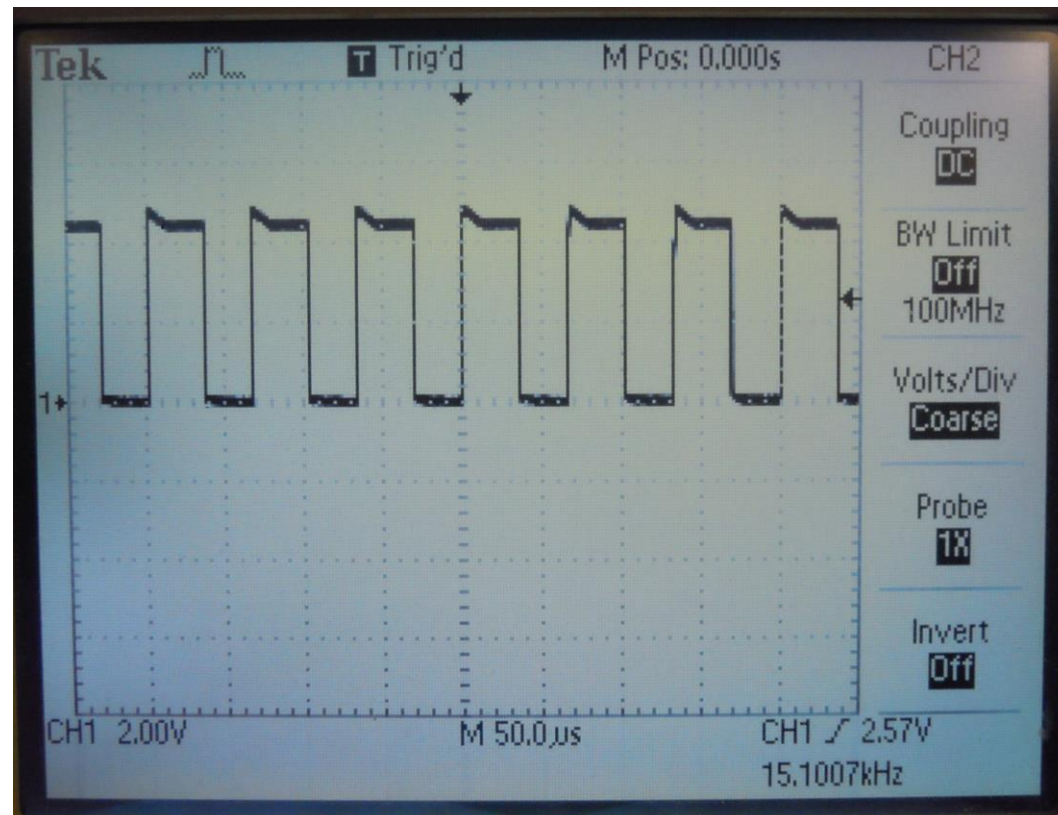
# WAVEFORM RECTIFICATION



- ❖ Unfortunately, the output of the pulse signal from NE555 is not always perfect.




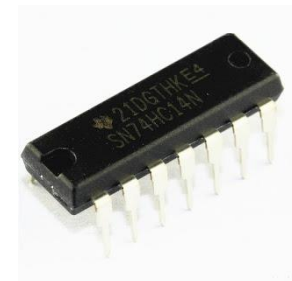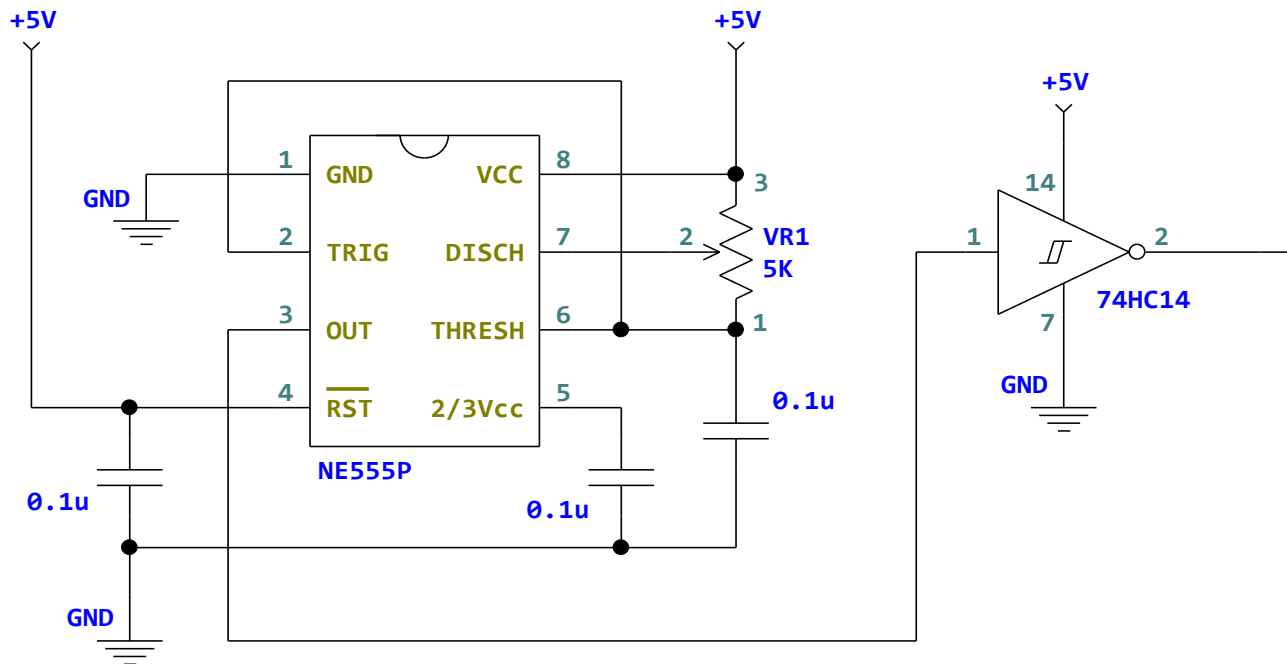
# SCHMITT TRIGGER [1]

- ❖ We can use Schmitt Trigger (**74HC14**) to rectify the waveform



1	14
2	13
3	12
4	11
5	10
6	9
7	8

## 74HC14









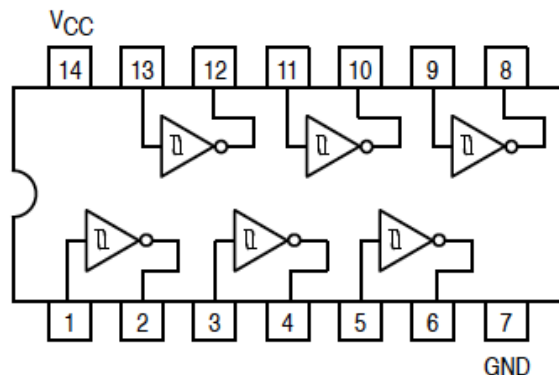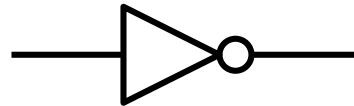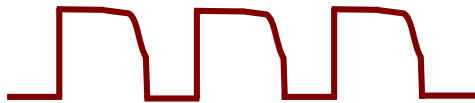
## SCHMITT TRIGGER [2]

- ❖ The output of 555 timer is re-shaped by the Schmitt Trigger (74HC14)




- The output is inverted
- There are 6 Schmitt Triggers and you only need to use one
- Even not shown, the  $V_{CC}$  (positive supply) and  $GND$  has to be connected to power for proper function


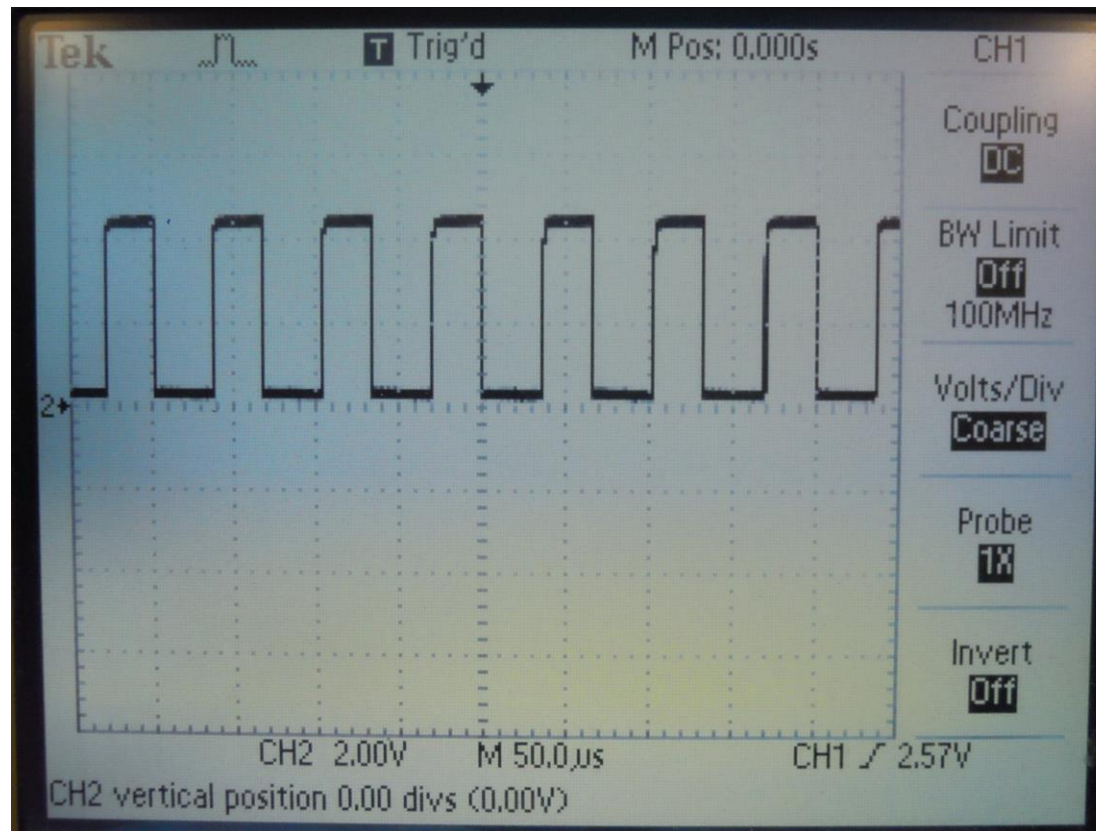
# SCHMITT TRIGGER [3]


- ❖ After going through the Schmitt trigger, the waveform is clean.




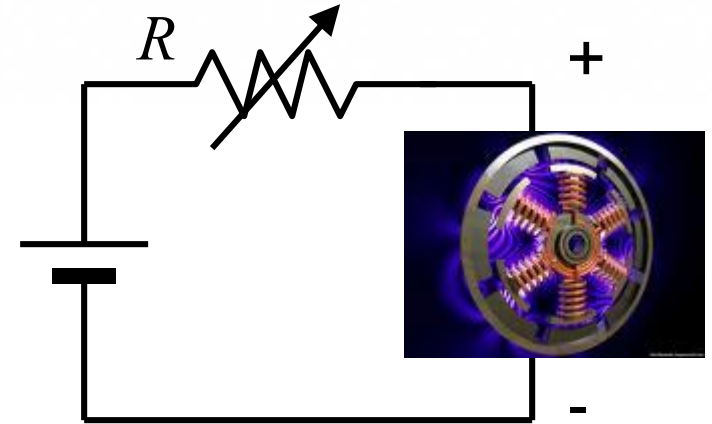
# GENERIC MOTOR SPEED CONTROL

- ❖ Higher voltage leads to larger current, higher power and faster rotation
- ❖ Different voltages can be obtained by using a variable resistor




## ❖ Disadvantages:

- It is difficult to control the speed precisely
- Need mechanical motion to tune the resistor and not computer friendly


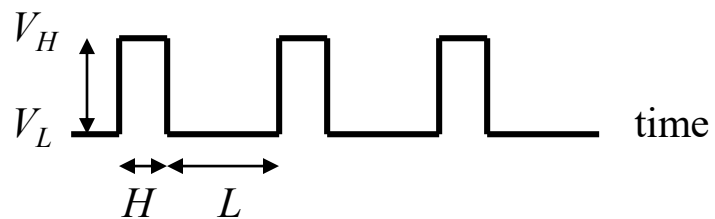
# LECTURE SUMMARY

- ❖ Motor Basic
- ❖ IC
- ❖ Pulse signal characteristics







# NEXT LECTURE

- ❖ Pulse Width Modulation (PWM)



QUESTIONS?

